

555 Timer Tone Generator

555 Timer
Astable

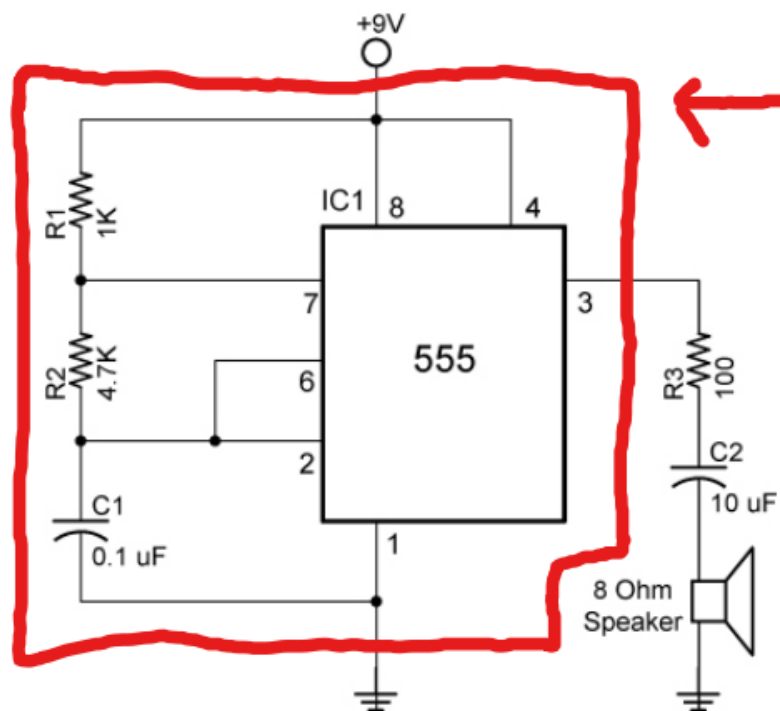


Figure 1 – 555 Timer Tone Generator


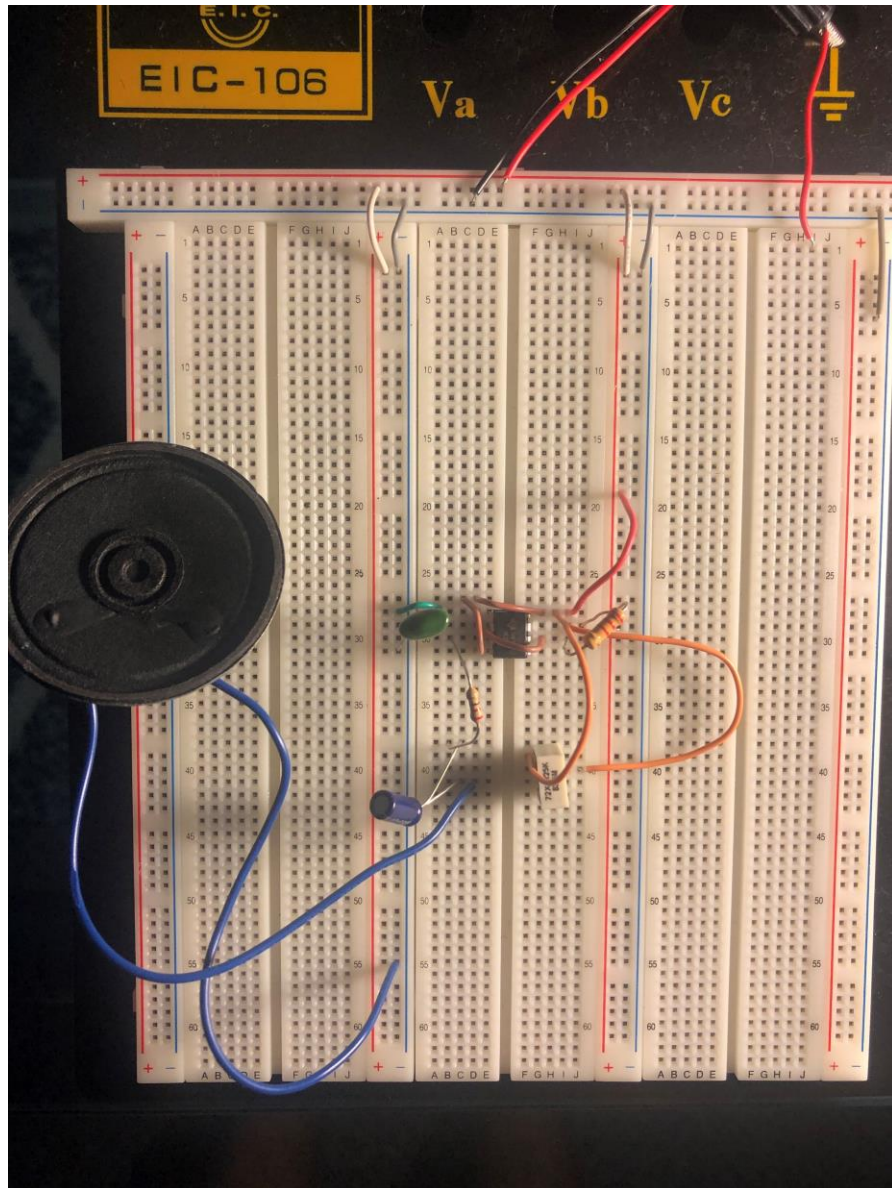


Figure 2 – 555 Timer Tone Generator Breadboard Verification

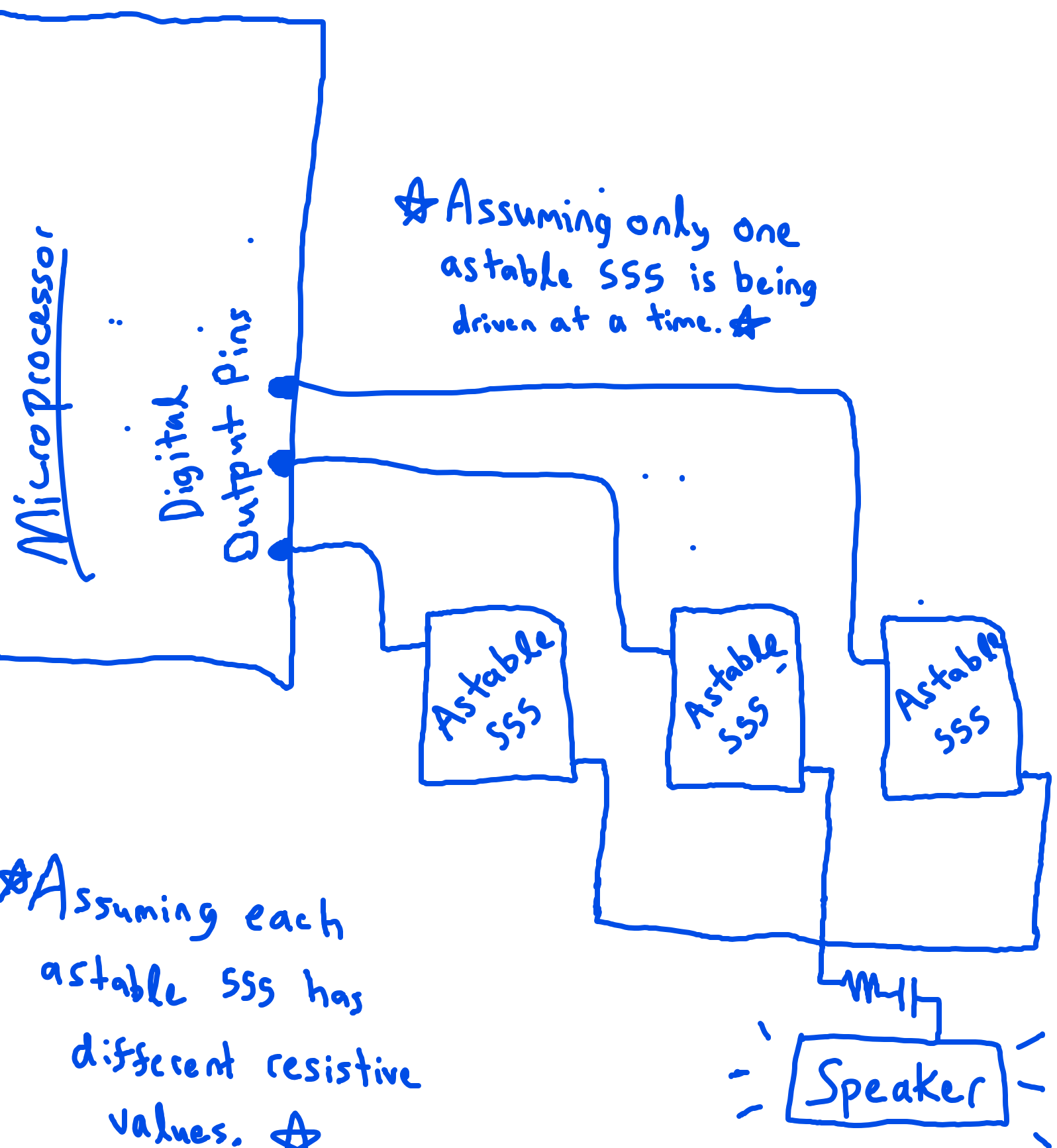

★ Assuming only one
astable SSS is being
driven at a time. ★

★ Assuming each
astable SSS has
different resistive
values. ★

Speaker